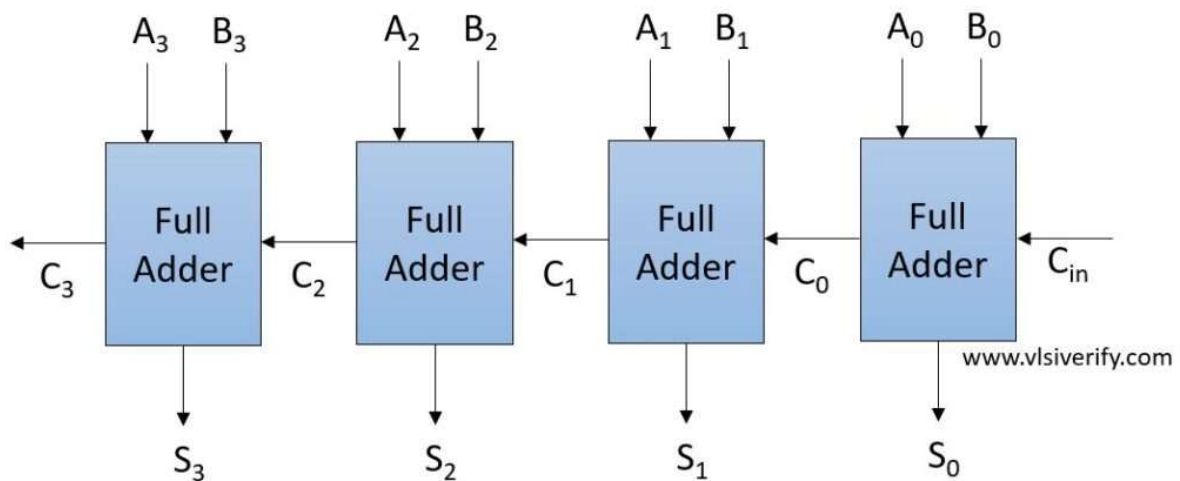


#50DAYS CHALLENGE

DAY 5

4 BIT RIPPLE CARRY ADDER

Block Diagram



4-Bit Ripple Carry Adder

a)Design Code

```
module full_adder(input a,b,c, output sum,carry);
    assign sum=a^b^c;
    assign carry=(a&b) | (a&c) | (b&c);
endmodule

module ripple_carry_adder(a,b,c,sum,carry);
    input [3:0]a,b;
    input c;
    output [3:0] sum;
    output carry;
    wire c1,c2,c3;

    full_adder f1(.a(a[0]),.b(b[0]),.c(c),.sum(sum[0]),.carry(c1));
    full_adder f2(.a(a[1]),.b(b[1]),.c(c1),.sum(sum[1]),.carry(c2));
    full_adder f3(.a(a[2]),.b(b[2]),.c(c2),.sum(sum[2]),.carry(c3));
    full_adder f4(.a(a[3]),.b(b[3]),.c(c3),.sum(sum[3]),.carry(carry));

endmodule
```

b) Testbench


```

module ripple_carry_adder_tb();
    reg [3:0] a,b;
    reg c;
    wire [3:0] sum;
    wire carry;
    integer i,j;

    ripple_carry_adder dut(a,b,c,sum,carry);
    initial
    begin
        c=0;
        for(i=0;i<16;i=i+1)
        begin
            for(j=0;j<16;j=j+1)
            begin
                a=i; b=j;
                #10;
                $display("Time=%t | a=%b |b=%b |c=%b |sum=%b |carry=%b", $time,a,b,c,sum,carry);
            end
            end
            c=1;
            for(i=0;i<16;i=i+1)
            begin
                for(j=0;j<16;j=j+1)
                begin
                    a=i; b=j;
                    #10;
                    $display("Time=%t | a=%b |b=%b |c=%b |sum=%b |carry=%b", $time,a,b,c,sum,carry);
                end
            end
        end
        $finish();
    end
endmodule

```

c) Waveform

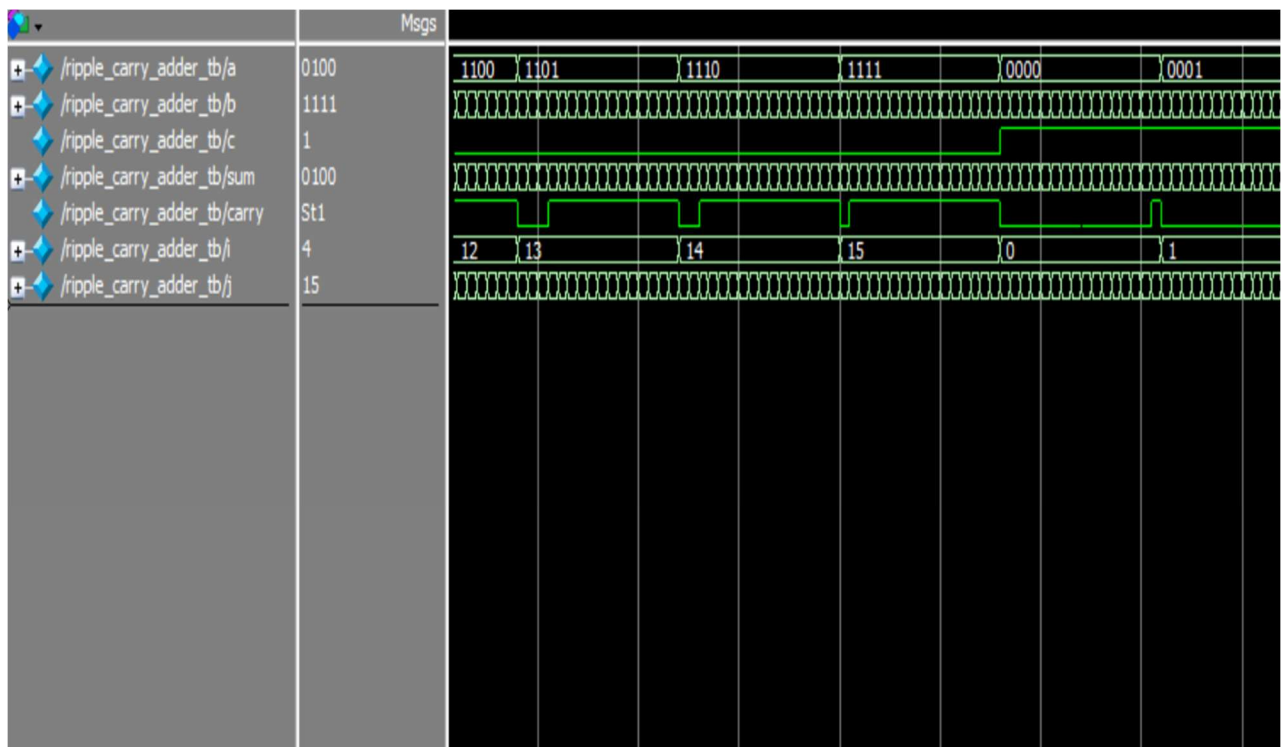

d) Console Output

```
# Time= 10 | a=0000 |b=0000 |c=0 |sum=0000 |carry=0
# Time= 20 | a=0000 |b=0001 |c=0 |sum=0001 |carry=0
# Time= 30 | a=0000 |b=0010 |c=0 |sum=0010 |carry=0
# Time= 40 | a=0000 |b=0011 |c=0 |sum=0011 |carry=0
# Time= 50 | a=0000 |b=0100 |c=0 |sum=0100 |carry=0
# Time= 60 | a=0000 |b=0101 |c=0 |sum=0101 |carry=0
# Time= 70 | a=0000 |b=0110 |c=0 |sum=0110 |carry=0
# Time= 80 | a=0000 |b=0111 |c=0 |sum=0111 |carry=0
# Time= 90 | a=0000 |b=1000 |c=0 |sum=1000 |carry=0
# Time= 100 | a=0000 |b=1001 |c=0 |sum=1001 |carry=0
# Time= 110 | a=0000 |b=1010 |c=0 |sum=1010 |carry=0
# Time= 120 | a=0000 |b=1011 |c=0 |sum=1011 |carry=0
# Time= 130 | a=0000 |b=1100 |c=0 |sum=1100 |carry=0
# Time= 140 | a=0000 |b=1101 |c=0 |sum=1101 |carry=0
# Time= 150 | a=0000 |b=1110 |c=0 |sum=1110 |carry=0
# Time= 160 | a=0000 |b=1111 |c=0 |sum=1111 |carry=0
# Time= 170 | a=0001 |b=0000 |c=0 |sum=0001 |carry=0
# Time= 180 | a=0001 |b=0001 |c=0 |sum=0010 |carry=0
# Time= 190 | a=0001 |b=0010 |c=0 |sum=0011 |carry=0
# Time= 200 | a=0001 |b=0011 |c=0 |sum=0100 |carry=0
# Time= 210 | a=0001 |b=0100 |c=0 |sum=0101 |carry=0
# Time= 220 | a=0001 |b=0101 |c=0 |sum=0110 |carry=0
# Time= 230 | a=0001 |b=0110 |c=0 |sum=0111 |carry=0
# Time= 240 | a=0001 |b=0111 |c=0 |sum=1000 |carry=0
# Time= 250 | a=0001 |b=1000 |c=0 |sum=1001 |carry=0
# Time= 260 | a=0001 |b=1001 |c=0 |sum=1010 |carry=0
# Time= 270 | a=0001 |b=1010 |c=0 |sum=1011 |carry=0
# Time= 280 | a=0001 |b=1011 |c=0 |sum=1100 |carry=0
# Time= 290 | a=0001 |b=1100 |c=0 |sum=1101 |carry=0
# Time= 300 | a=0001 |b=1101 |c=0 |sum=1110 |carry=0
# Time= 310 | a=0001 |b=1110 |c=0 |sum=1111 |carry=0
# Time= 320 | a=0001 |b=1111 |c=0 |sum=0000 |carry=1
# Time= 330 | a=0010 |b=0000 |c=0 |sum=0010 |carry=0
# Time= 340 | a=0010 |b=0001 |c=0 |sum=0011 |carry=0
# Time= 350 | a=0010 |b=0010 |c=0 |sum=0100 |carry=0
```